

Emergency Panic Alarm Board

BY: Harshita Panwar


Schematic diagram:

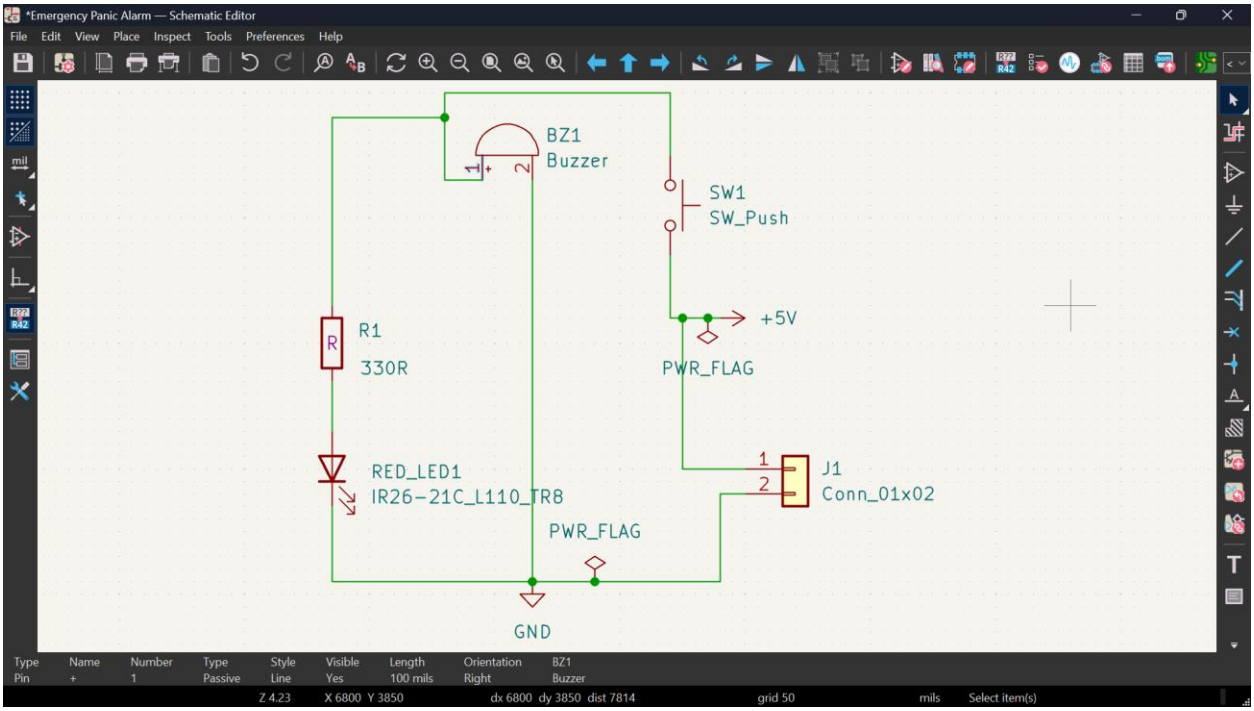

2D PCB View Screenshot:

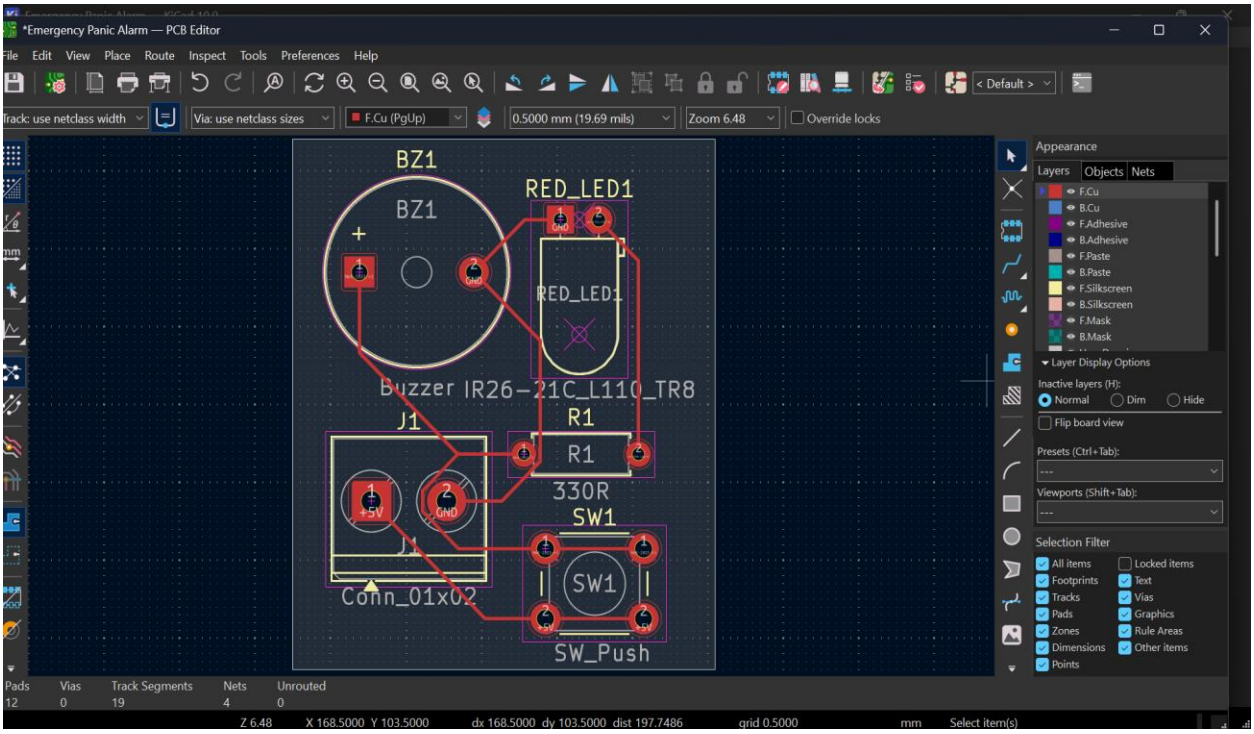

3D PCB View Screenshot:

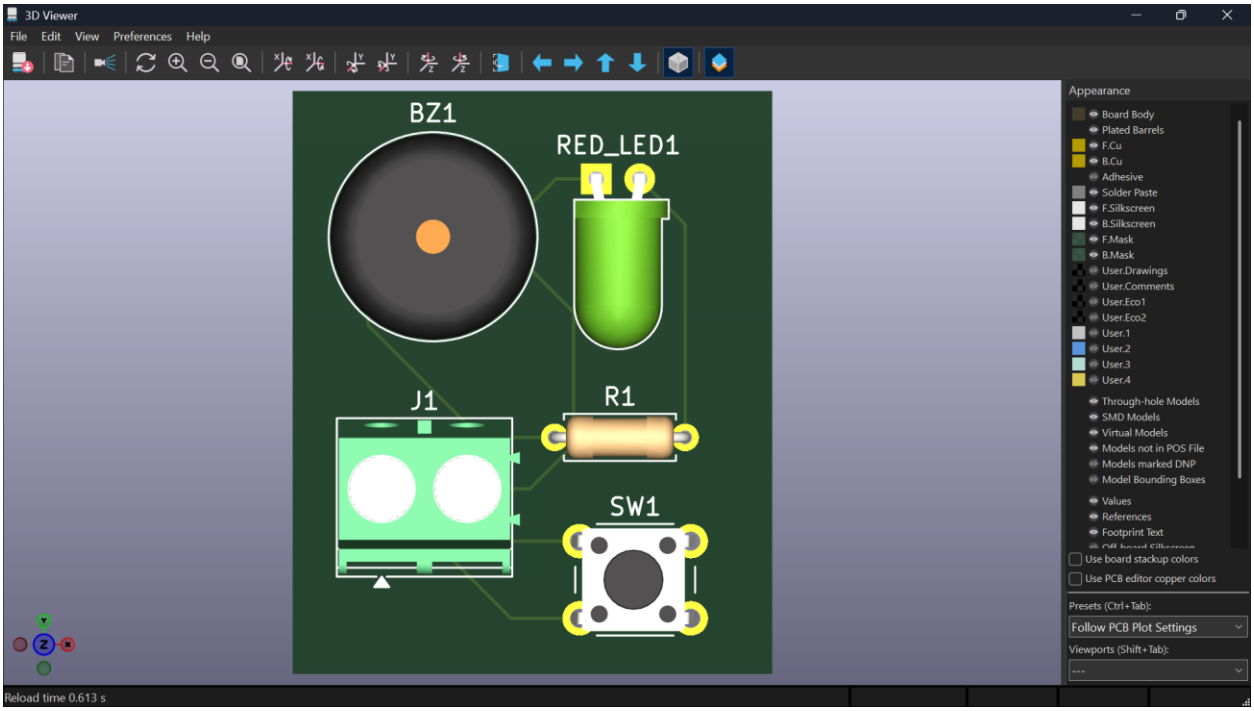

Bill Of Materials (BOM):

Reference Designator	Qty	Component / Value	Footprint / Package	Description
J1	1	`Conn_01x02`	`TerminalBlock_Phoenix_PT-1,5-2-5.0-H`	2-pin screw terminal for 5V power input
SW1	1	Push Button	`SW_PUSH_6mm`	6mm tactile push switch (alarm trigger)
BZ1	1	Active Buzzer	`Buzzer Beeper`	5V active sounder/buzzer
R1	1	`330Ω`	`R Axial`	Current-limiting resistor (1/4W)

Reference Designator	Qty	Component / Value	Footprint / Package	Description
D1	1	Red LED	`LED_D5.0mm`	5mm through-hole red LED